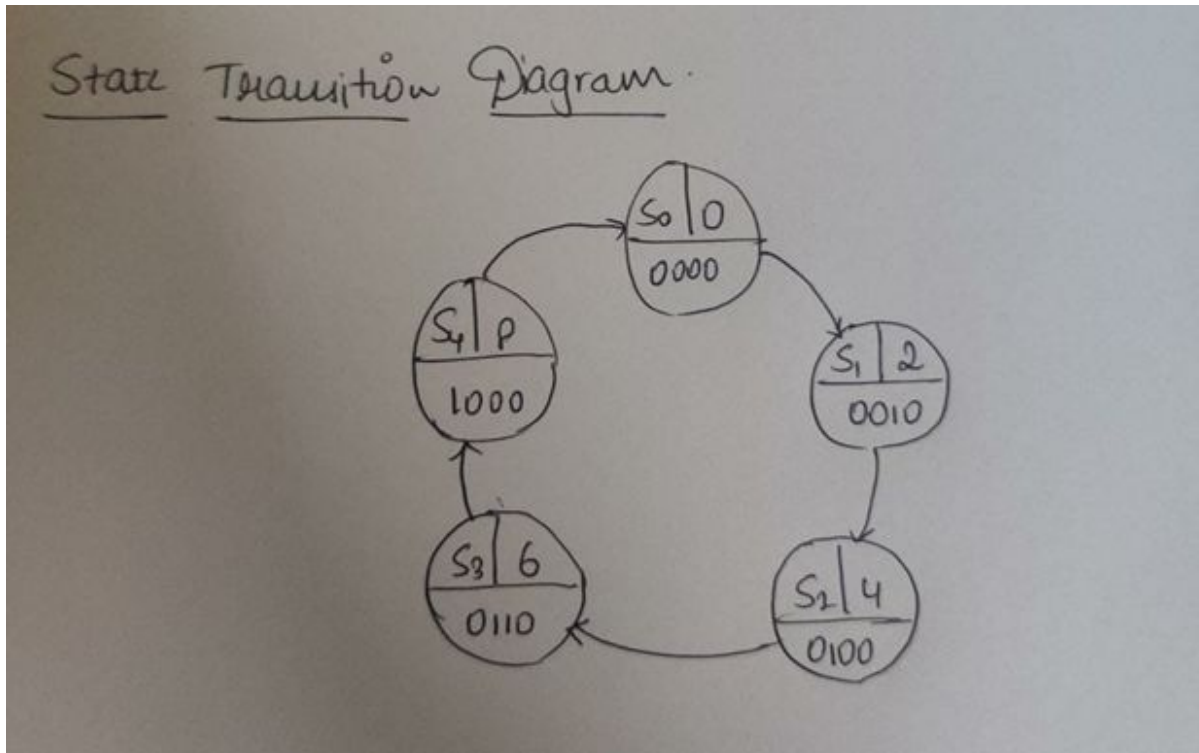


Problem Statement: Design & implement a sequence generator.(Even number generator- 0,2,4,6,8)

State Transition Diagram:



Since the Least Significant Bit in all the states is zero because the numbers are even, we eliminate the need for a flip flop for the LSB bit of each number generated.

State Transition Table:

Present State	Next State
S ₀	S ₁

S ₁	S ₂
S ₂	S ₃
S ₃	S ₄
S ₄	S ₀

State Encodings:

State	S0	S1	S2
S ₀	0	0	0
S ₁	0	0	1
S ₂	0	1	0
S ₃	0	1	1
S ₄	1	0	0

State Transition Table(with Encodings):

S0	S1	S2	S0'	S1'	S2'
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0

Solving for S0',S1',S2', we get:

$$S0' = S0 \oplus S1 \oplus S2$$

$$S1' = S0 \oplus (S1 \oplus S2)$$

$$S2' = S0 \oplus S2$$

